

Code: 9A04404

B.Tech II Year II Semester (R09) Supplementary Examinations December/January 2014/2015

**PULSE & DIGITAL CIRCUITS**

(Common to ECE, EIE, E.Con.E, ECC & MCT)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions  
All questions carry equal marks

\*\*\*\*\*

- 1 (a) Explain the response of a high pass circuit, if an exponential input is applied.  
(b) Write short note on piping process.
- 2 (a) What is meant by clipping in wave shaping?  
(b) Classify different types of clipper circuits. Give their circuits and explain their operation with the aid of transfer characteristics.
- 3 Write short notes on:  
(a) Diode switching times.  
(b) Switching characteristics of transistors.  
(c) FET as a switch.
- 4 Explain about various switching conditions of Schmitt trigger.
- 5 (a) What are sweep circuits?  
(b) Explain how you generate a saw tooth waveform with a neat circuit diagram.
- 6 (a) Explain the operation of series and shunt FET sampling gates.  
(b) What are the advantages of FET sampling gates over transistor sampling gates?
- 7 How synchronization and frequency division are related? What are the methods used for synchronization of monoshot circuit?
- 8 (a) What is the difference between floating and grounded inputs?  
(b) Design and explain the concept of discrete type of gates.

\*\*\*\*\*